

Smart Thermostat

You want to design a smart thermostat that intelligently manages whether an HVAC unit is heating or cooling to improve the efficiency of a home.

Inputs

You have access to the switch to the power supply of an HVAC unit X , which you can write as

$$X = \begin{cases} 0 & \text{when power of HVAC (heating or cooling) is off} \\ 1 & \text{when power of HVAC (heating or cooling) is on.} \end{cases} \quad (1)$$

When the thermostat reaches a comfort temperature, it reports this through the logical signal T . You can write this signal as

$$T = \begin{cases} 0 & \text{when temperature} < \text{comfort}^\circ \\ 1 & \text{otherwise.} \end{cases} \quad (2)$$

You want to design the system to only heat or cool to the comfort temperature when motion is detected, which is reported by a motion sensor's logic signal M ,

$$M = \begin{cases} 0 & \text{last motion detected} > 30\text{min ago} \\ 1 & \text{last motion detected} < 30\text{min ago.} \end{cases} \quad (3)$$

Outputs

Now, you need your thermostat to report whether the HVAC is operating in heating or cooling mode. You define two new logic signals, C and H , as your *outputs* which you write as

$$C = \begin{cases} 1 & \text{set HVAC in cooler mode} \\ 0 & \text{otherwise,} \end{cases} \quad H = \begin{cases} 1 & \text{set HVAC in heater mode} \\ 0 & \text{otherwise.} \end{cases}$$

Problem 1 ($2 \times 4 = 8$ points possible)

1. Derive logic functions that implement the cooling and heating output signals C and H for your Smart Thermostat.
2. Create a truth table for the system. Use signals X, T, M as input and signals C, H as output. Indicate the number of possible inputs for this system (i.e., the number of rows of the truth table).
3. Draw gate-level schematics for the output signals C and H .
4. Define a new output signal

$$Y = \begin{cases} 1 & \text{HVAC is operating in either cooler or heater mode} \\ 0 & \text{HVAC is not operating.} \end{cases}$$

Derive the simplest possible expression for Y .

Problem 1 Solution:

Part 1

We want to heat the house when the temperature falls *below* the comfort temperature, i.e. $\bar{T} = 1$. So, we conclude

$$H = X \cdot M \cdot \bar{T}, \quad C = X \cdot M \cdot T.$$

Part 2

There are $2^3 = 8$ possible inputs. The truth table takes the following form.

X	T	M	\bar{T}	C	H
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	0	1	0

Part 3

Lots of variants of the logic gate diagrams are accepted.

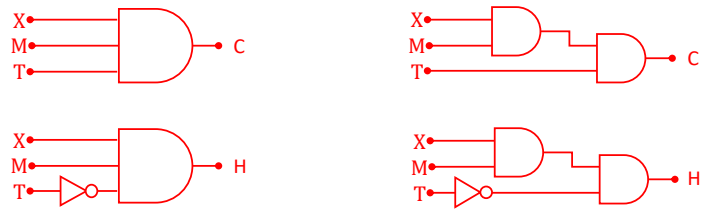


Figure 1: The smart thermostat system

Part 4

We have

$$\begin{aligned}
 Y &= C + H \\
 &= XM(T + \bar{T}) \\
 &= XM \cdot 1 = XM,
 \end{aligned}$$

where we used $T + \bar{T} = 1$.

Fun With Schematics

Problem 2 ($2 \times 4 = 8$ points possible)

Consider the following two logic functions. Draw both

1. gate-level schematics, and
2. switch logic schematics,

without simplifying the expressions. Do not use complemented variables, e.g., \overline{A} as inputs; instead, draw the NOT gates or normally-closed switches in the schematic.

$$F_1 = (A \cdot B) + C \cdot (A + B) + C \cdot A + B \quad (4a)$$

$$F_2 = \overline{A} + AB + \overline{C}D\overline{A} + \overline{C}D \quad (4b)$$

Problem 2 solution:

F_1 schematics

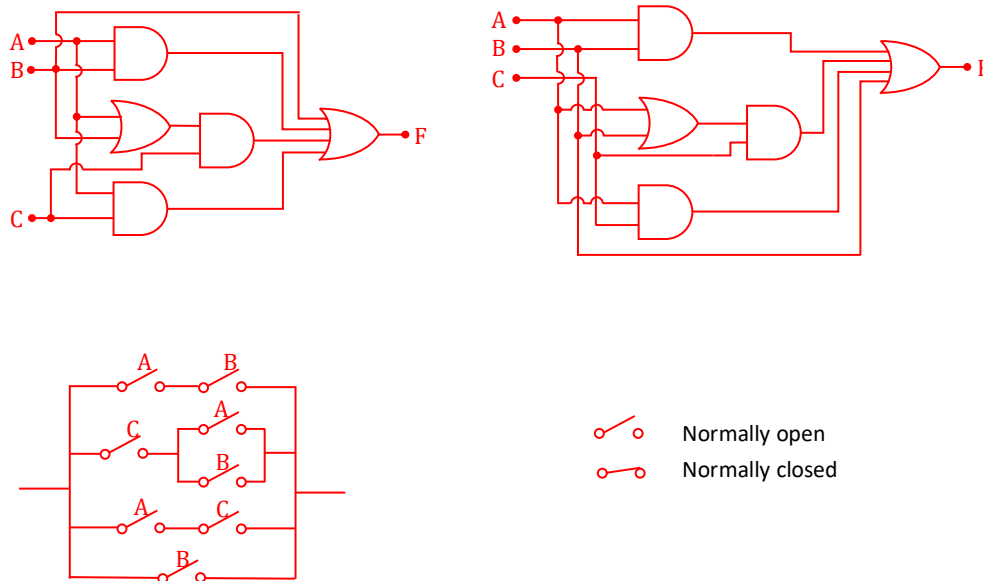


Figure 2: The F_1 switching and logic schematics

F_2 schematics

$$F = \bar{A} + AB + \bar{C}D\bar{A} + \bar{C}D$$

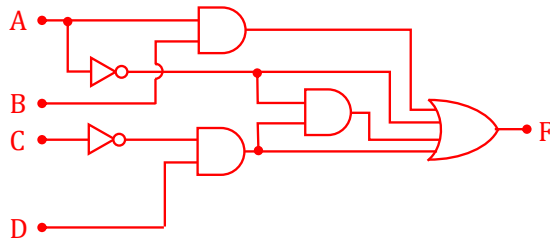


Figure 3: The F_2 switching and logic schematics

Boolean Algebra

Study the *Boolean Identities* document on Canvas.

Problem 3 ($2 \times 2 = 4$ points possible)

Derive the simplest possible forms of the following logic functions, providing each step of your derivation. *No need to draw the circuits.*

$$F_1 = (A \cdot B) + C \cdot (A + B) + C \cdot A + B \quad (5a)$$

$$F_2 = \overline{A} + AB + \overline{C}D\overline{A} + \overline{C}D \quad (5b)$$

Problem 3 Solution:

F_1

We have that

$$\begin{aligned} F_1 &= (A \cdot B) + C \cdot (A + B) + C \cdot A + B \\ &= AB + CA + CB + CA + B \\ &\stackrel{(1)}{=} AB + CA + CB + B \\ &\stackrel{(2)}{=} AB + CA + B \\ &\stackrel{(3)}{=} B + CA. \end{aligned}$$

where step (1) is by noting that $CA + CA = CA$, step (2) is by absorption: $CB + B = B$, and step (3) is by absorption again: $AB + B = B$.

F_2

We obtain

$$\begin{aligned} F_2 &= \overline{A} + AB + \overline{C}D\overline{A} + \overline{C}D \\ &= \overline{A} + AB + \overline{C}D(\overline{A} + 1) \\ &= \overline{A} + AB + \overline{C}D \\ &\stackrel{(1)}{=} \overline{A} \underbrace{(B + 1)}_{=1} + AB + \overline{C}D \\ &\stackrel{(2)}{=} \overline{A} + B \underbrace{(\overline{A} + A)}_{=1} + \overline{C}D \\ &\stackrel{(3)}{=} \overline{A} + B + \overline{C}D \end{aligned}$$

where in step (1) we introduce an AND with $(B + 1)$ without changing anything, and in step (2) we apply the distributive property and factor. The result in step (3) is known as the *disappearing opposite* theorem: $\overline{A} + AB = \overline{A} + B$, or equivalently, $A + \overline{A}B = A + B$.