


Agenda:

- Recapping material for Exam 2
- General complements
- sequential $\rightarrow$ Nonidempotencies

- $\rightarrow$ Adders
- $\rightarrow$ Decoders/Encoders
- $\rightarrow$ Multiplexers/Demultiplexers

Exam: Oct 17th - Oct 19th

Up next:

- State Machines
- Latches
- Low-level

- Number systems
- Building blocks


Exam guidelines:

- Please do not collaborate on the first pass
- Generative AI - let me know how you used it (if you did)
- You're responsible for the output

Recap: Decoders

$\rightarrow$ Turns binary input into the index of an output signal in base 10

$2 \Rightarrow 4$

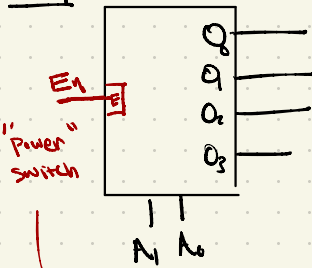

For each i , $O_i = 1$ if $((A_1 A_0)_2)_{10} = i$

4 rows that we don't care about

E_n	A_1	A_0	O_3	O_2	O_1	O_0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


Predetermined to 1

$A_1 A_0$
 $(1\ 0)_2 = 2$

Enable signal

A_1	A_0	O_3	O_2	O_1	O_0
0	0				
0	1				
1	0		E_n		
1	1	E_n		E_n	


DeMultiplexers (e.g. "1 to 4")

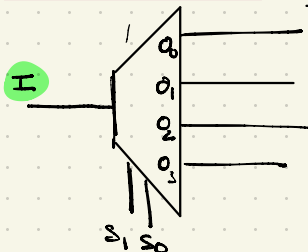

The enable is the input to DEMUX


Multiplexers - Selects one of many inputs

eg. $4 \rightarrow 1$

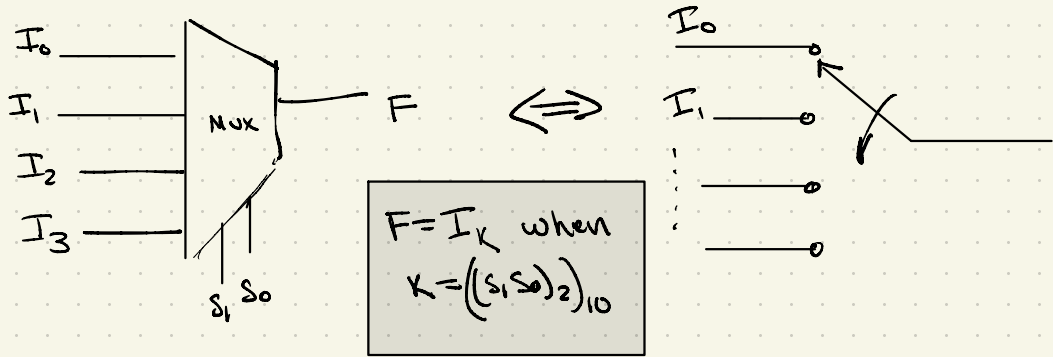

S_1	S_0	I_3	I_2	I_1	I_0	F
0	0	0	0	0	I_0	I_0
0	1	0	0	I_1	0	I_1
1	0	0	I_2	0	0	I_2
1	1	I_3	0	0	0	I_3

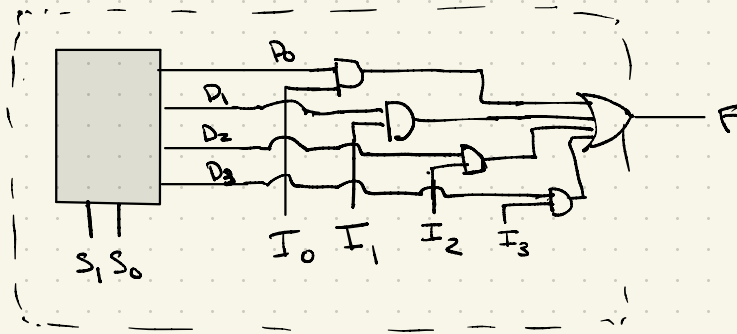
Relationship between Decoders & Multiplexers



$$\begin{aligned}
 F &= D_0 I_0 + D_1 I_1 + D_2 I_2 + D_3 I_3 \\
 &= \underbrace{\bar{S}_1 \bar{S}_0}_{\text{"00"}} I_0 + \underbrace{\bar{S}_1 S_0}_{\text{"01"}} I_1 + \underbrace{S_1 \bar{S}_0}_{\text{"10"}} I_2 + \underbrace{S_1 S_0}_{\text{"11"}} I_3
 \end{aligned}$$

Example:

1 → 8 De multiplexer

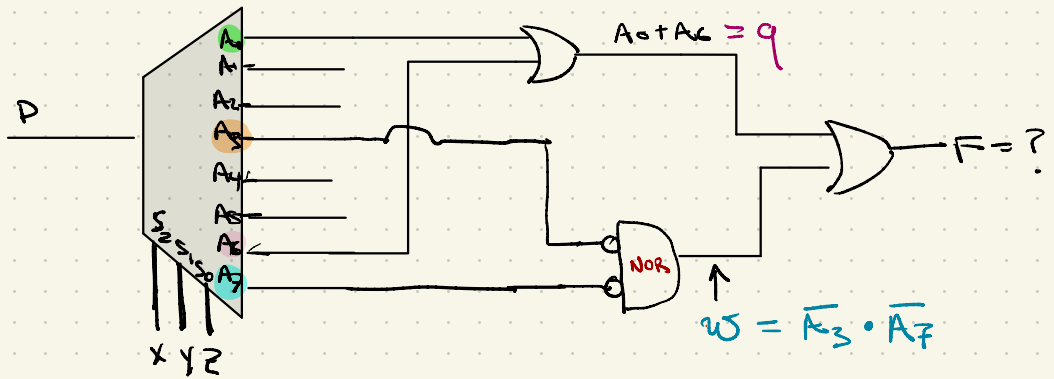

$$A_0 = \overline{x} \cdot \overline{y} \cdot \overline{z} \quad A_6 = x \cdot y \cdot \overline{z}$$

$$A_3 = \overline{x} \cdot y \cdot \overline{z} \quad A_7 = x \cdot y \cdot z$$

$$F = w + q \triangleq \overline{A_3} \cdot \overline{A_7} + A_0 + A_6$$



$$= (\overline{x \cdot y \cdot z}) \cdot (\overline{x \cdot y \cdot z}) + \overline{x} \cdot \overline{y} \cdot \overline{z} + x \cdot y \cdot \overline{z}$$

De Morgan

(FOIL)

$$= (x + y + z) \cdot (\overline{x} + \overline{y} + \overline{z}) + \overline{x} \cdot \overline{y} \cdot \overline{z} + x \cdot y \cdot \overline{z}$$

$$= \cancel{x}x + x\overline{y} + x\overline{z} + \overline{y} \cdot \overline{x} + \overline{y} + \overline{z} + \overline{x}\overline{y}\overline{z} + x\overline{y}\overline{z}$$

$$= \cancel{x} + \overline{z} + \cancel{\overline{y}} + \overline{x}\overline{y}\overline{z} + x\overline{y}\overline{z}$$

$$= \overline{y} + \overline{z} + \overline{x}\overline{y}\overline{z} + x\overline{y}\overline{z}$$

$$= \overline{y} + \overline{z}(1 + \cancel{\overline{x}\overline{y}}) + x\overline{y}\overline{z}$$

$$= \overline{y} + \overline{z} + x\overline{y}\overline{z}$$

$$= \overline{y} + \overline{z}$$



16's Complement Question (Challenge Question)

$$X = (D_{n-1} D_{n-2} \dots D_1 D_0)_b = \sum_{k=0}^{n-1} D_k b^k$$

B length $4n$ (base 2) $\longleftrightarrow$ H

ex $B = \underbrace{1011}_{(B)} \underbrace{0011}_{(3)}_{16}$

Hex # $= (11)_{10}$

$n=2$

$$B = (\beta_{n-1} \beta_{n-2} \dots \beta_0)$$

$$B = \sum_{k=0}^{4n-1} \beta_k 2^k = \sum_{k=0}^{n-1} h_k \cdot 16^k$$

Ones' Complement of B

$$-B = 1^{4n} - \sum_{k=0}^{4n-1} \beta_k 2^k$$